
EE 371 HW2

- 1. a. Number of words: 2^8 = 256, number of bits per word : 8
 - b. Number of words: $2^9 = 512$, number of bits per word: 6

2.

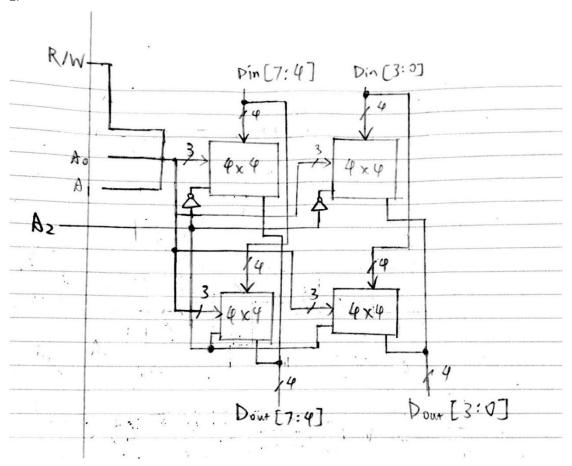


3. a. one chip is 8M * 16 / 8 = 16M bytes

64M / 16M = 4

4 chips are needed

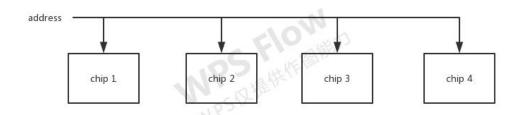By connecting all chips in series, I can get a total capacity of 8M * 64, which is 64M bytes




- b. $8M = 2^{3}*2^{20} = 23$ bits
- c. All of these bits are connected to the address input
- d. 0 bits


4.




5.

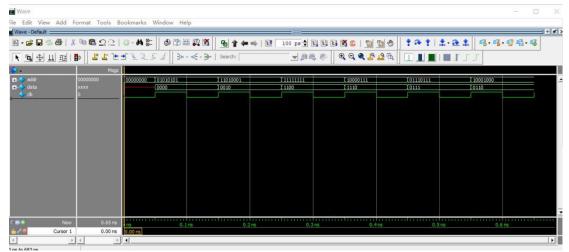


4 bit ROM simulation

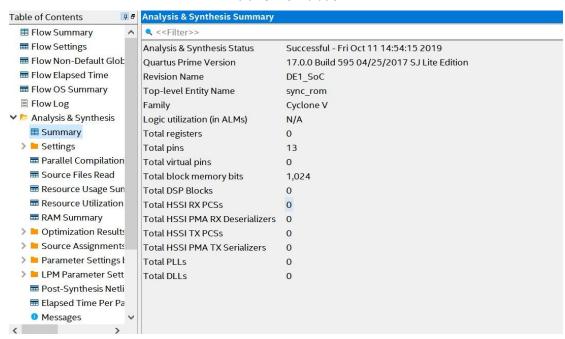

4 bit ROM synthesis report

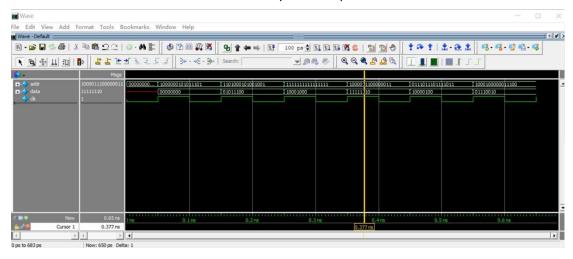


8 bit ROM simulation

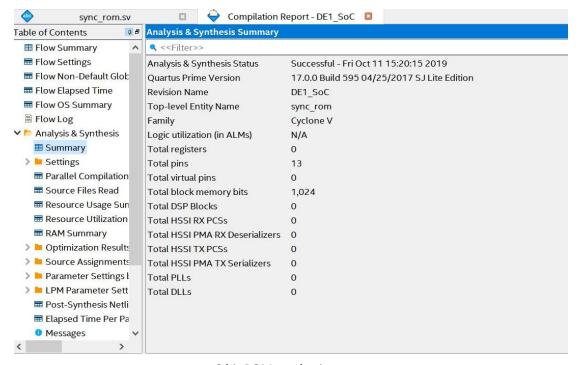

8 bit ROM synthesis report

Size of question 4:9

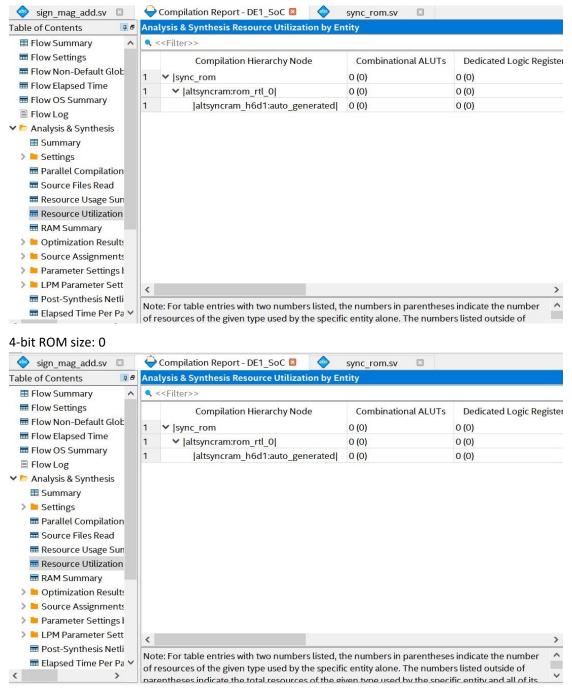

8-bit ROM size: 0

Feedback

In this homework I had some trouble understanding the questions. Some questions are not very specific. For instance, question 3 did not mention how we should connect the chips. I also had much trouble working on question 5 since I did not know how to run simulation when reading from txt files.